

<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)



Likes: 0



Dislikes: 0

## Expert Answer

### General Guidance

The answer provided below has been developed in a clear step by step manner. Step: 1

#### To find:

% change in length of the beam =  $\frac{\Delta L}{L} \times 100$

#### Given values:


- Gauge factor of strain gauge = **S = 2.1**
- Output of difference amplifier = **V<sub>out</sub> = 2 V**
- Resistance of undeformed strain gauge = **R = 120 Ω**
- Excitation voltage of bridge = **E = 10 V**

#### Assignments:

- V1 = Input to negative terminal of op-amp
- V2 = Input to positive terminal of op-amp
- V0 = Output of strain gauge = V2 - V1 (since output of strain gauge is fed as input to difference amplifier as shown in Fig. 1 below)
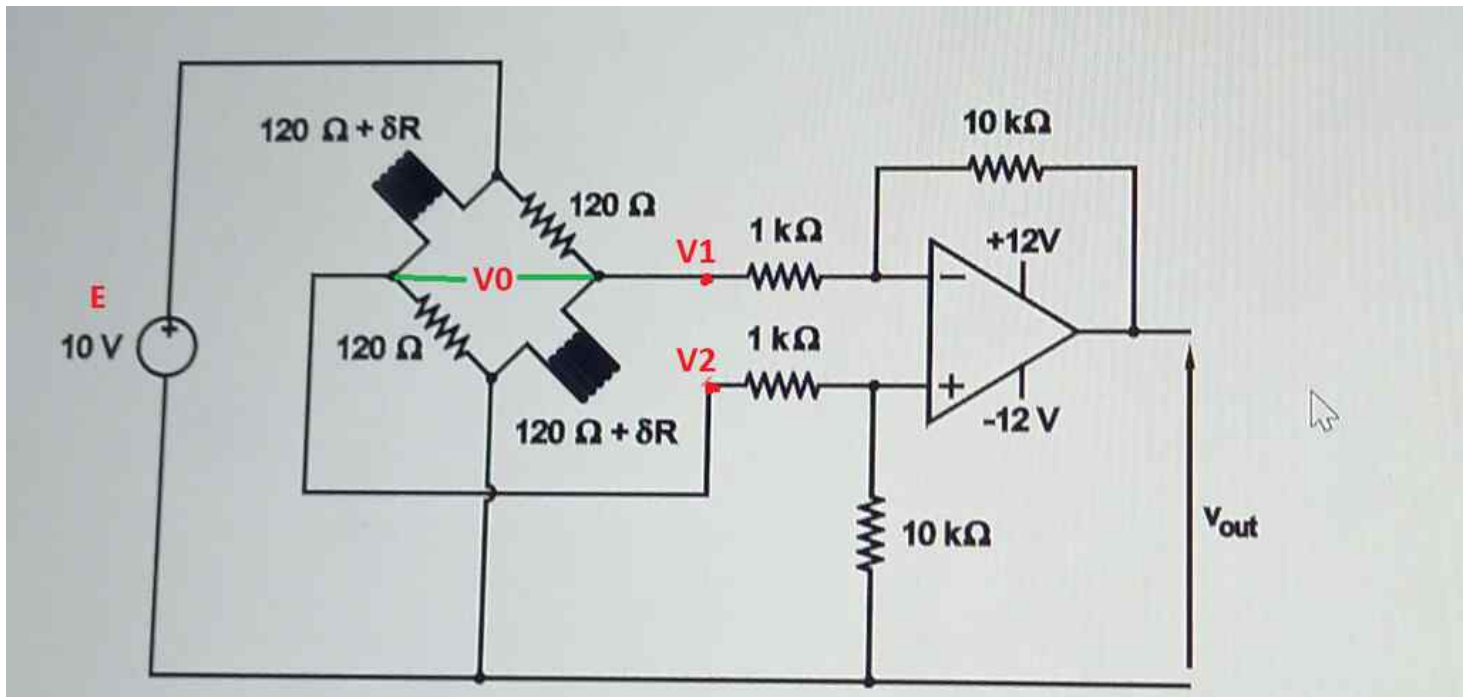
#### Explanation of circuit:


- Two strain gauges are connected to form a bridge circuit.
- Bridge circuit is excited by E = 10 V
- Output of bridge circuit V0 is amplified to V<sub>out</sub> by using a difference amplifier based on op-amp



Explanation: Please refer to solution in this step. Step: 2

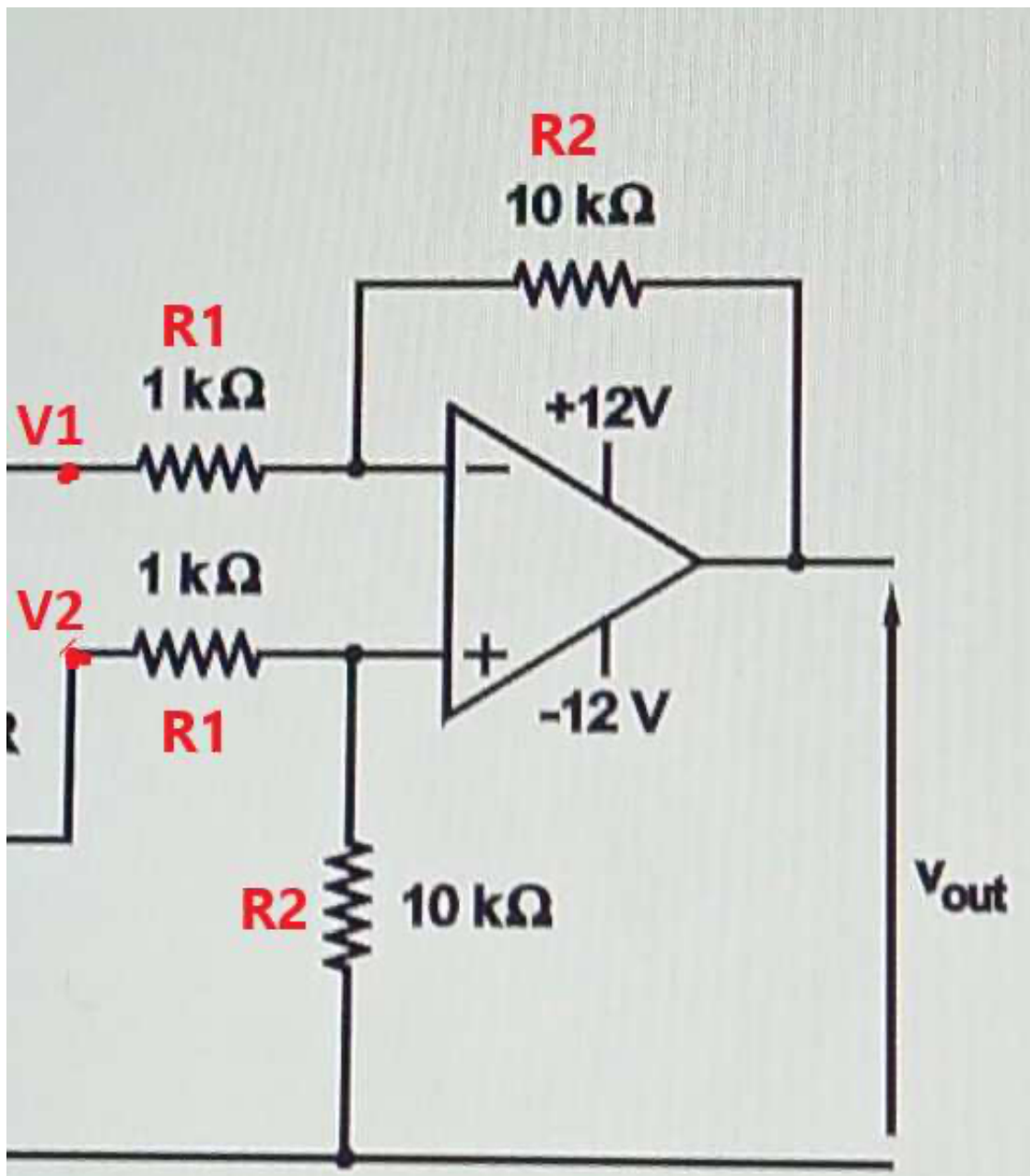**Step 1: Calculation of differential input of Difference amplifier ( $V_2 - V_1$ )**

Circuit of op-amp as difference amplifier is shown in Fig. 2 below:



Equation of a Differential amplifier is given by Eq. 1 below:

$$v_{out} = \left( \frac{R_2}{R_1} \right) \times (V_2 - V_1)$$

This is re-written as:

$$(V_2 - V_1) = \left( \frac{R_1}{R_2} \right) \times v_{out}$$


$$(V_2 - V_1) = \left( \frac{1k\Omega}{10k\Omega} \right) \times 2V$$

$$= 0.2V$$

Explanation: Please refer to solution in this step. Step: 3
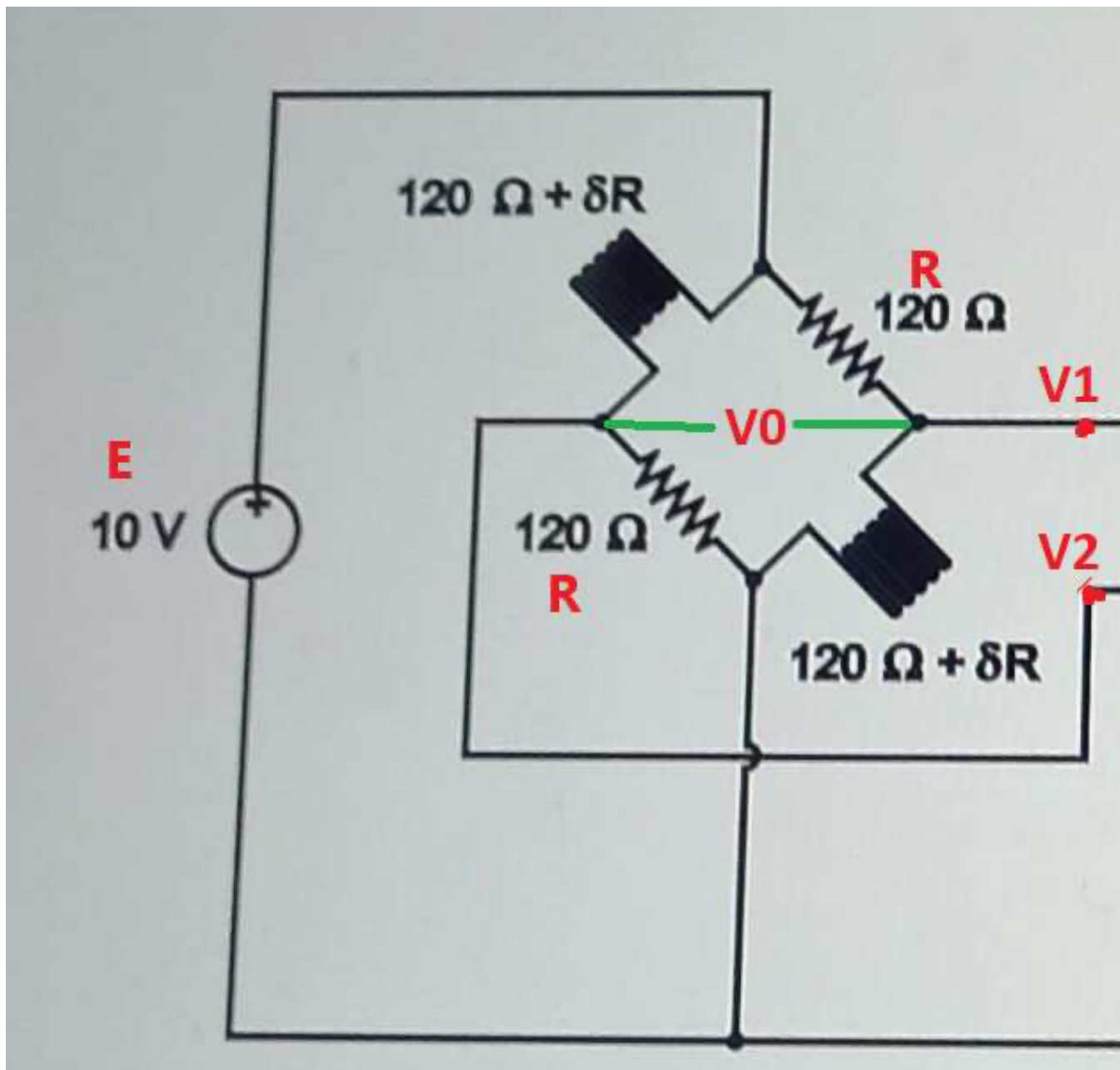
### **Step 2: Calculation of change in resistance of Strain gauge ( $\delta R$ )**

Circuit of bridge circuit is shown in Fig. 3 below:



Equation of the bridge circuit is given by Eq. 2 below:

$$V_0 = \left( \left( \frac{R}{2R + \delta R} \right) - \left( \frac{R + \delta R}{2R + \delta R} \right) \right) \times E$$

$$V_0 = \left( \frac{-\delta R}{2R + \delta R} \right) \times E$$

Substituting known values, we get

$$V_0 = \left( \frac{-\delta R}{(2 \times 120\Omega) + \delta R} \right) \times 10V$$

Since, Output voltage of bridge circuit is fed as input to difference amplifier, we can write

**$V_0 = V_2 - V_1 = 0.2 \text{ V}$**  (Ref. step 1) in the above equation

Hence, the equation becomes

$$0.2 = \left( \frac{-\delta R}{(2 \times 120) + \delta R} \right) \times 10$$

Solve this equation to obtain 'Change in resistance of strain gauge'  $\delta R$

$\delta R = -4.7\Omega$  (i.e., the strain gauge resistance decreased by  $4.7\Omega$ )

Explanation: Please refer to solution in this step. Step: 4

**Step 3: Calculate 'Percentage deflection of L' ( $\frac{\delta L}{L} \times 100$ )**

Equation of gauge factor (S) of strain gauge is given by Eq. 3 below:

$$S = \begin{pmatrix} \delta_R^R \\ \delta_L^L \end{pmatrix}$$

This is re-written as:

$$\frac{\Delta_L^L}{L} = \frac{\Delta_R^R}{S}$$

Hence, Percentage change in length is:

$$\frac{\delta_L^L}{L} \times 100 = \frac{\delta_R^R}{S} \times 100$$

$$= \frac{4.70}{120} \times 100$$

$$= 1.87 \%$$

$$\approx 1.9 \%$$

**Thus, the beam was deflected approximately by 1.9 % of L**

Explanation: Please refer to solution in this step.

**Answer:**

**Thus, the beam got deflected approximately by 1.9 % percentage of L**